


# **Digital Logic VI: Designing a 2-bit CPU**

CMSC 313


Sections 01, 02
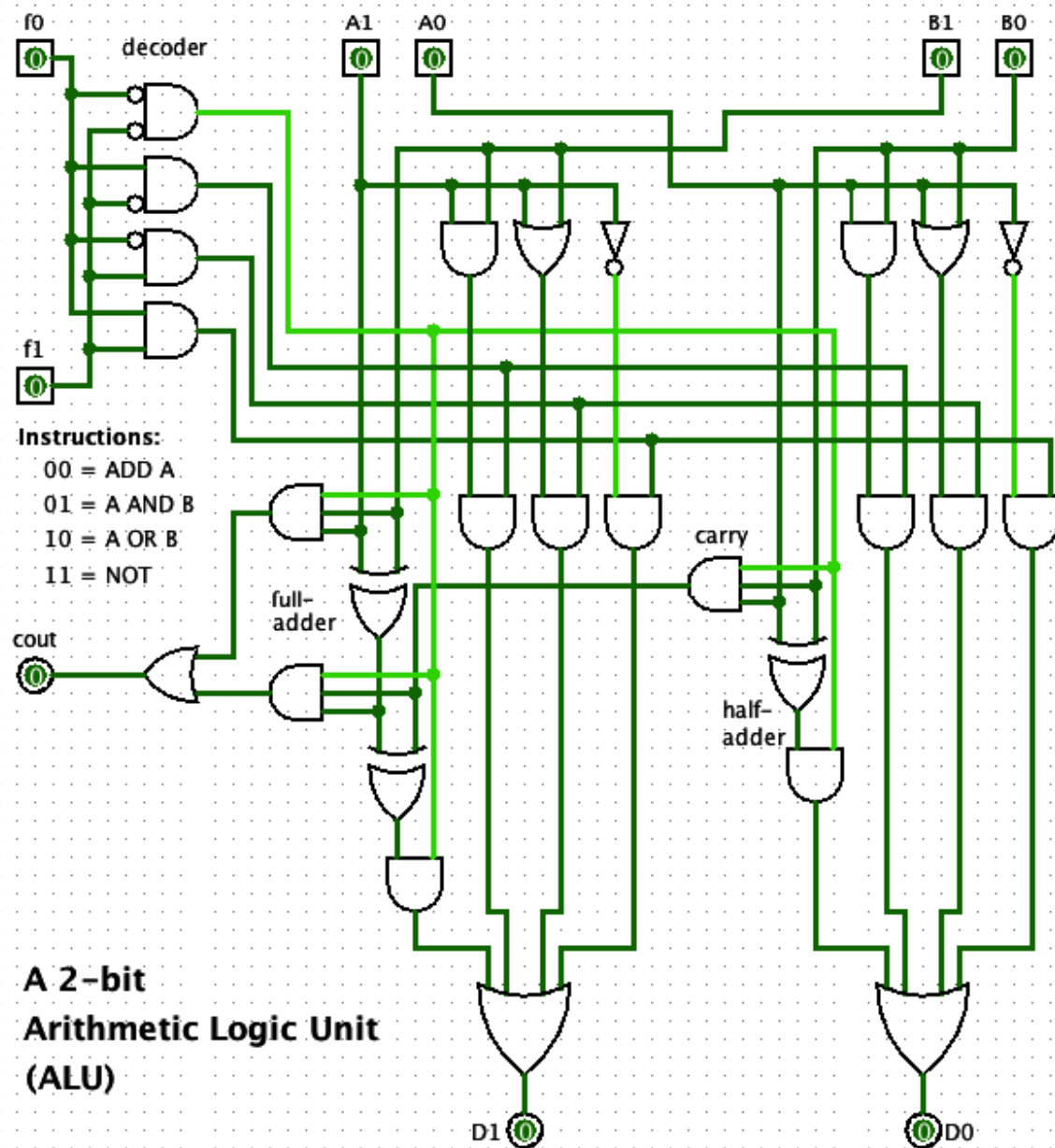
# 2-bit CPU: Version 1

- **2-bit ALU in sub-circuit**
- **Connect two 2-bit registers to 2-bit ALU**
- **Output of ALU stored in Register 1**




## 2-bit CPU, version 1

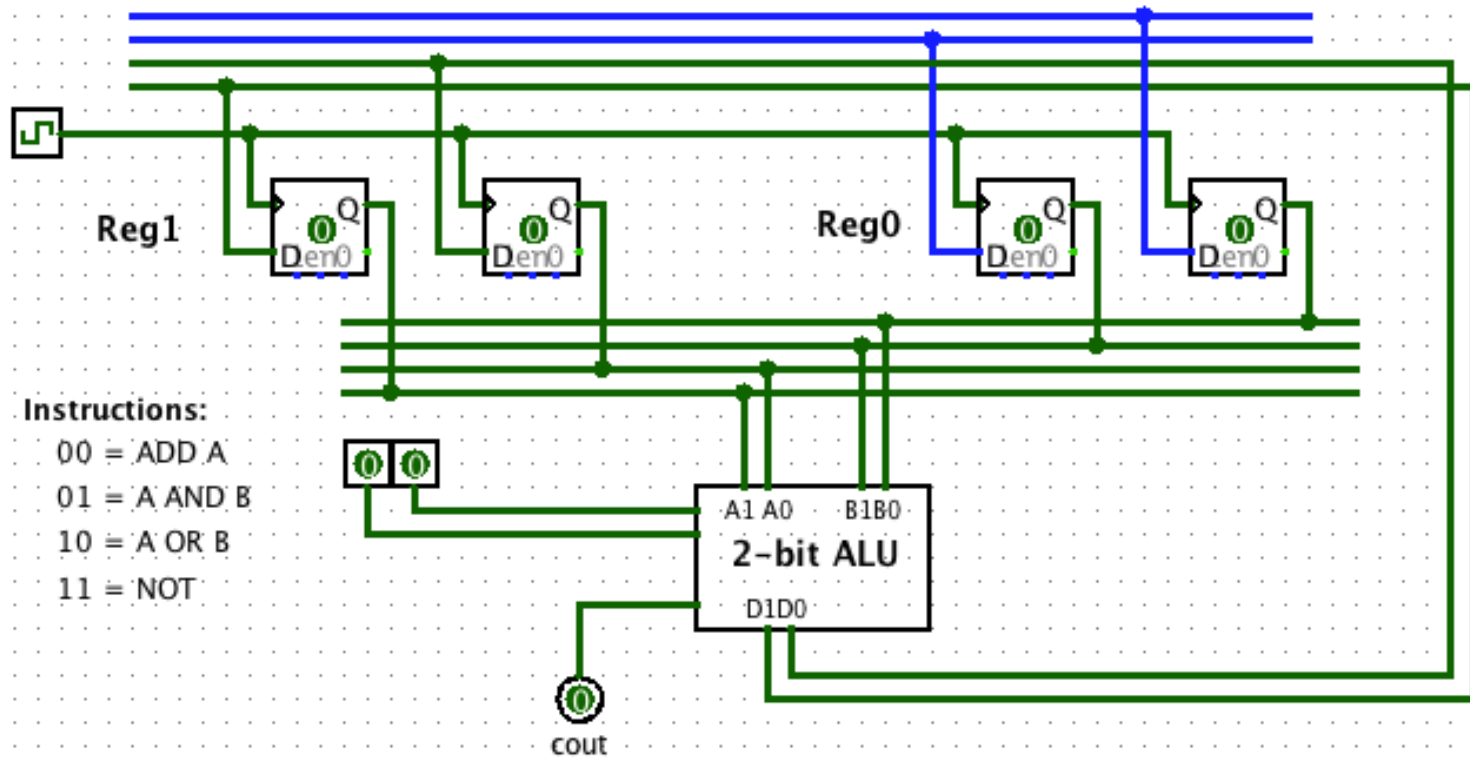

## 2-bit CPU: Version 2

- **Use DEMUX to select destination register**
- **Use Logisim wire bundles**


## 2-bit CPU, version 2

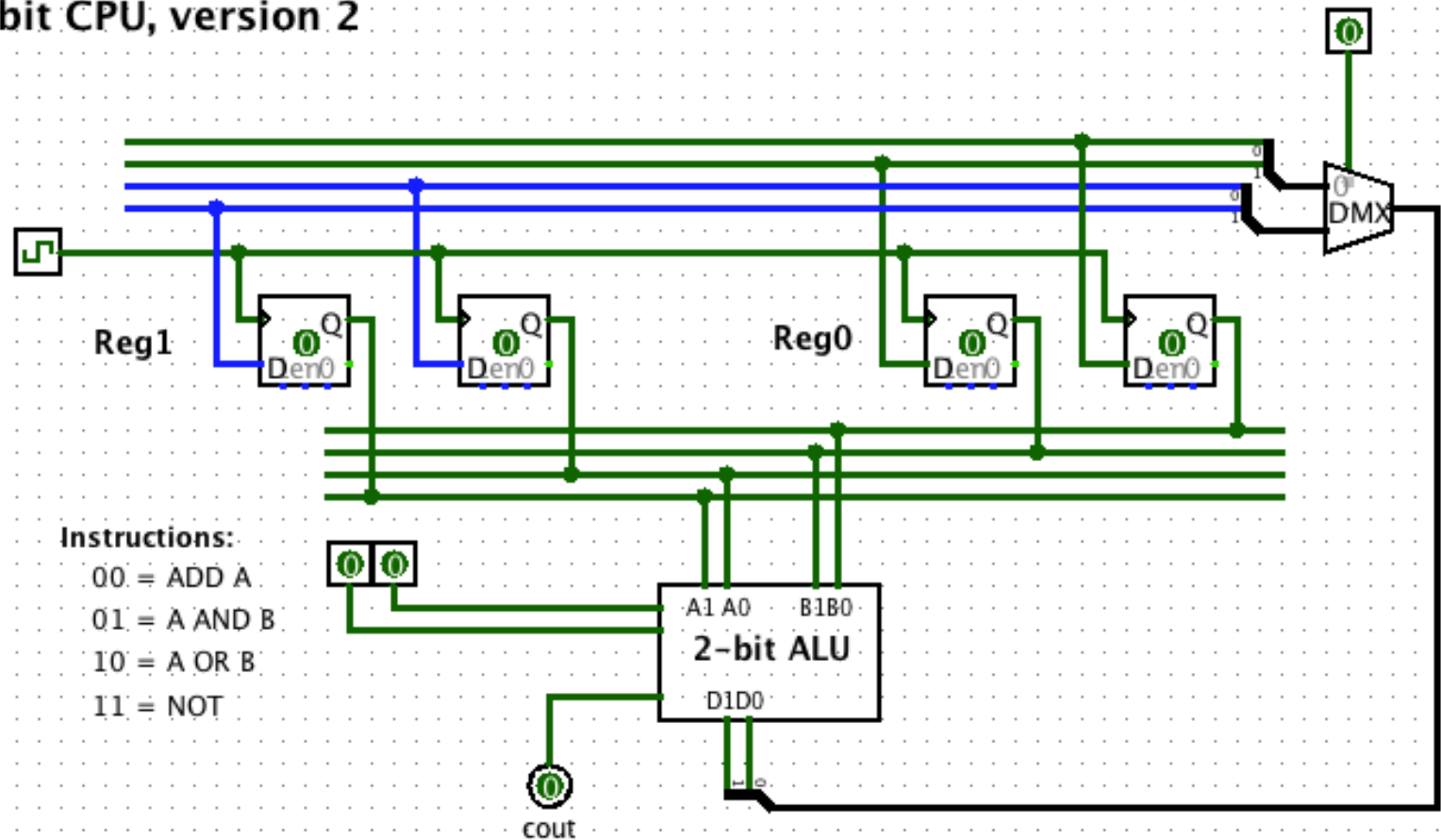

## 2-bit CPU: Version 3

**Use MUX to select input to each ALU "port".**

## 2-bit CPU, version 3

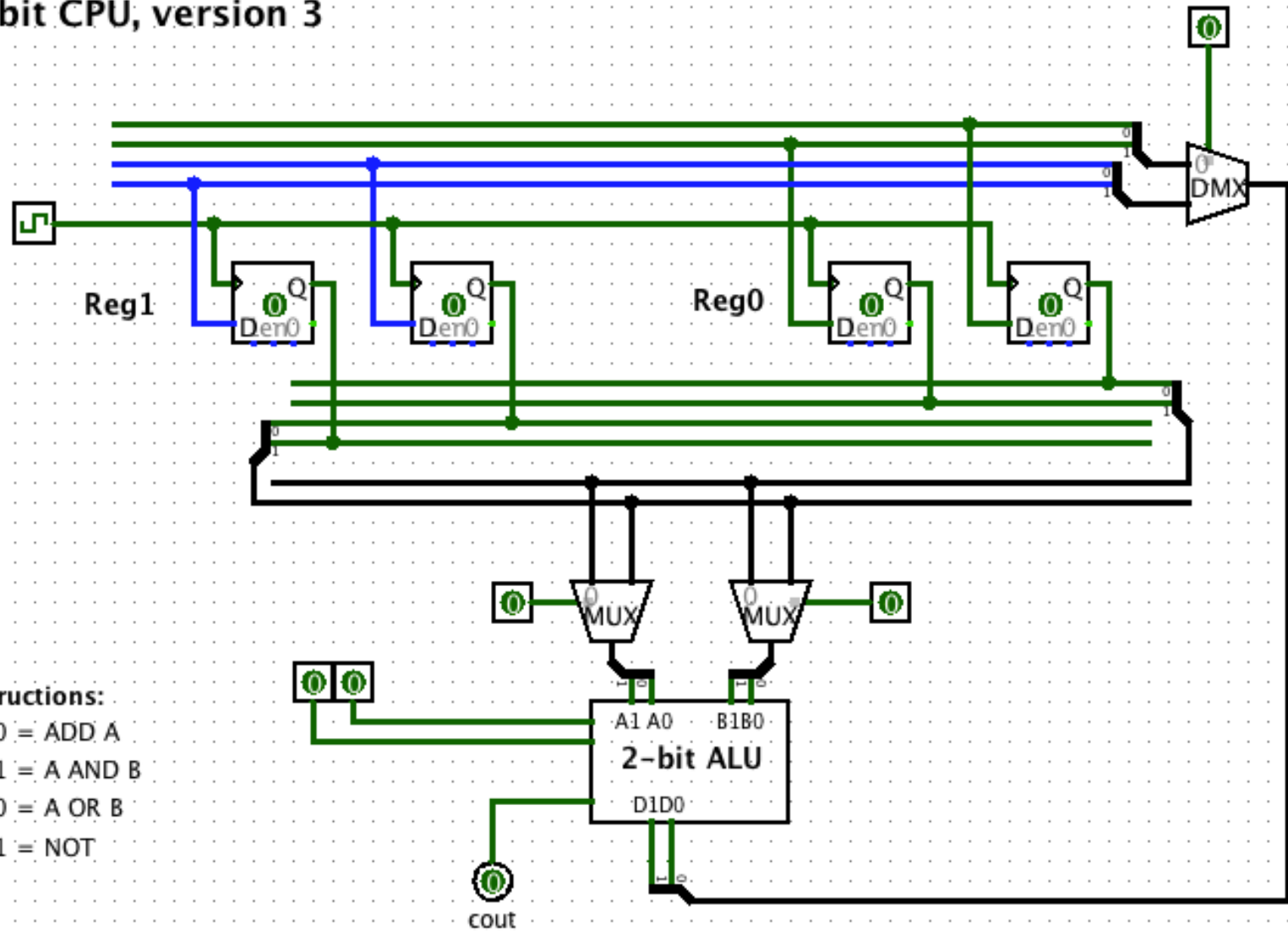




## 2-bit CPU: Version 4

- **Simplify "data bus" using wire bundles**
- **Add immediate operand to data bus**
- **Use result MUX to select input to DEMUX for destination register. Input may be:**
  - Register 0
  - Register 1
  - Immediate Operand
  - ALU output



# 2-bit CPU: Version 5

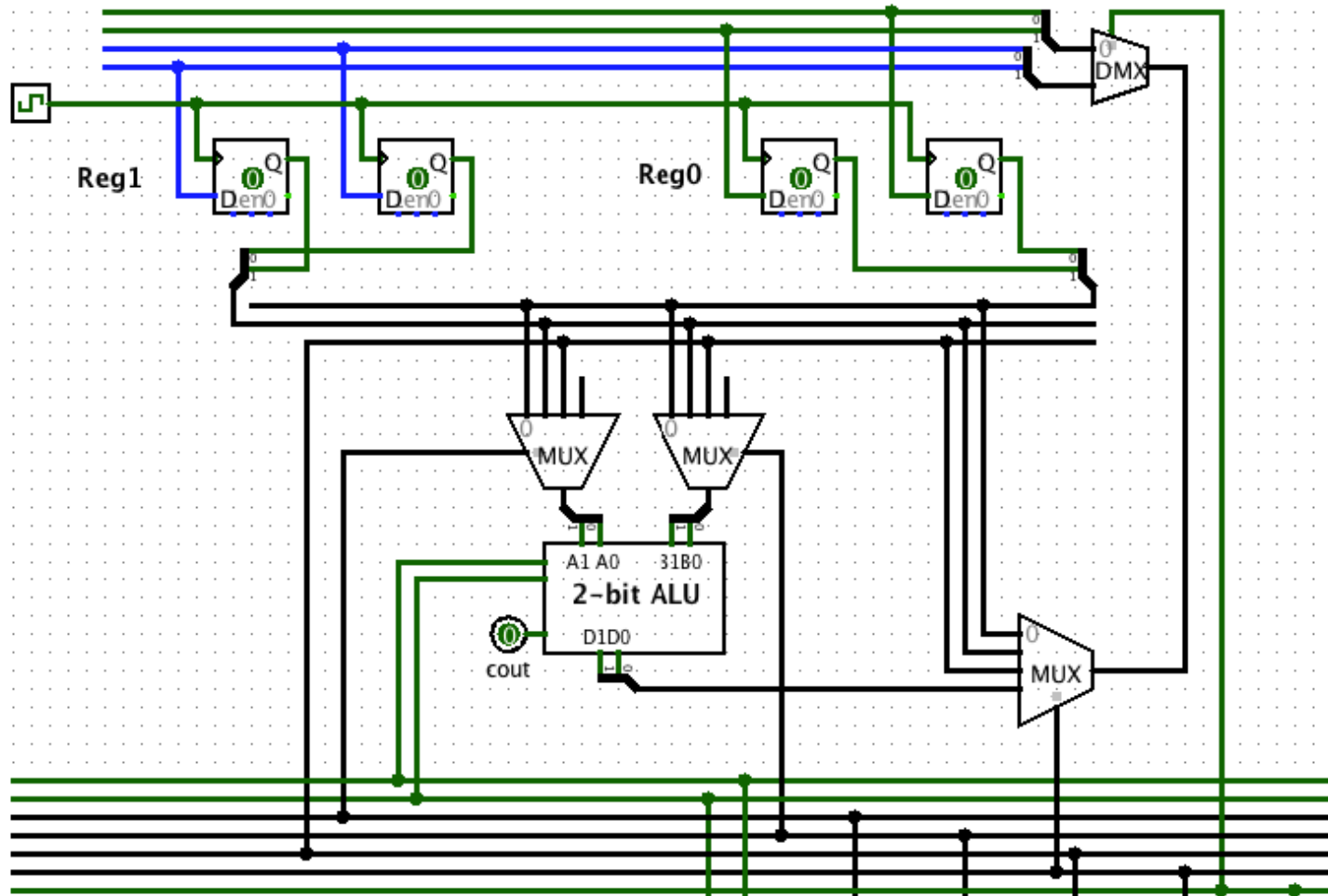**Consolidate controls to a "control bus"**



## 2-bit CPU, version 5


ALU Instructions:

00 = ADD A

01 = A AND B


10 = A OR B

11 = NOT

 

# 2-bit CPU: Version 6

Use 8-bit "instruction code"

 

- i7:** 0 if ALU instruction, 1 otherwise
- i6 i5:** ALU instruction
- i4:** operand 1 register (Reg 0 or Reg 1)
- i3 i2 i1:** 0rx = operand 2 is Reg r  
1xy = immediate operand xy
- i0:** destination register

# 2-bit CPU: Version 6

Use 8-bit "instruction code"

i7	i6	i5	i4	i3	i2	i1	i0
1	0	0	0				

- i7:** 0 if ALU instruction, 1 otherwise
- i6 i5 i4:** 000 = move, others not implemented
- i3 i2 i1:** 0rx = source operand is Reg r  
1xy = immediate operand xy
- i0:** destination register

# Instruction Decoder

## MUX for ALU port B

$$B1 = i3$$

$$\begin{aligned} B0 &= \overline{i3} i2 \overline{i1} + \overline{i3} i2 i1 \\ &= \overline{i3} i2 \end{aligned}$$

i3	i2	i1	B1	B0	
0	0	0	0	0	} Reg 0
0	0	1	0	0	
0	1	0	0	1	} Reg 1
0	1	1	0	1	
1	0	0	1	0	} Imm
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	0	

# Instruction Decoder


## Result MUX control

$$M1 = \overline{i7} + i3$$

$$M0 = \overline{i7} + \overline{i3} i2$$

i7	i3	i2	i1	M1	M0	
0	0	0	0	1	1	ALU
0	0	0	1	1	1	
0	0	1	0	1	1	
0	0	1	1	1	1	
0	1	0	0	1	1	
0	1	0	1	1	1	
0	1	1	0	1	1	
0	1	1	1	1	1	
1	0	0	0	0	0	Reg0
1	0	0	1	0	0	
1	0	1	0	0	1	Reg1
1	0	1	1	0	1	
1	1	0	0	1	0	Imm
1	1	0	1	1	0	
1	1	1	0	1	0	
1	1	1	1	1	0	



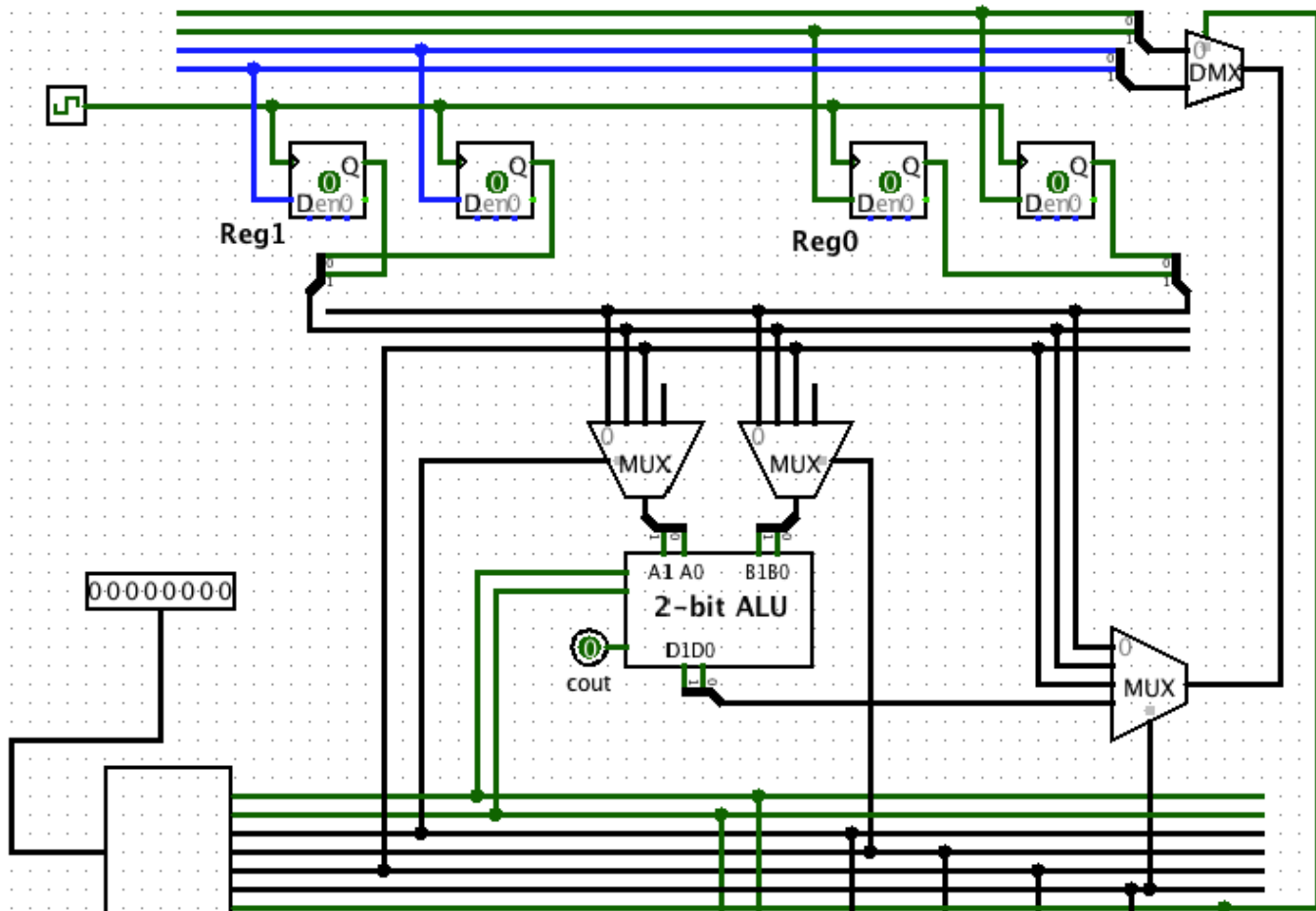

00000000

Instr. Decode

### 2-bit CPU, version 6

#### ALU Instructions:

- 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT


0
0
0
0
0
1
1
0

ALU inst    ALU A    ALU B    imm    Res MUX    dest

**ALU MUX**                      **RES MUX**  
 00=Reg0 01=Reg1    00=Reg0 01=Reg1  
 10=imm 11=xx        10=imm 11=ALU

00000000


# Instruction Decoder

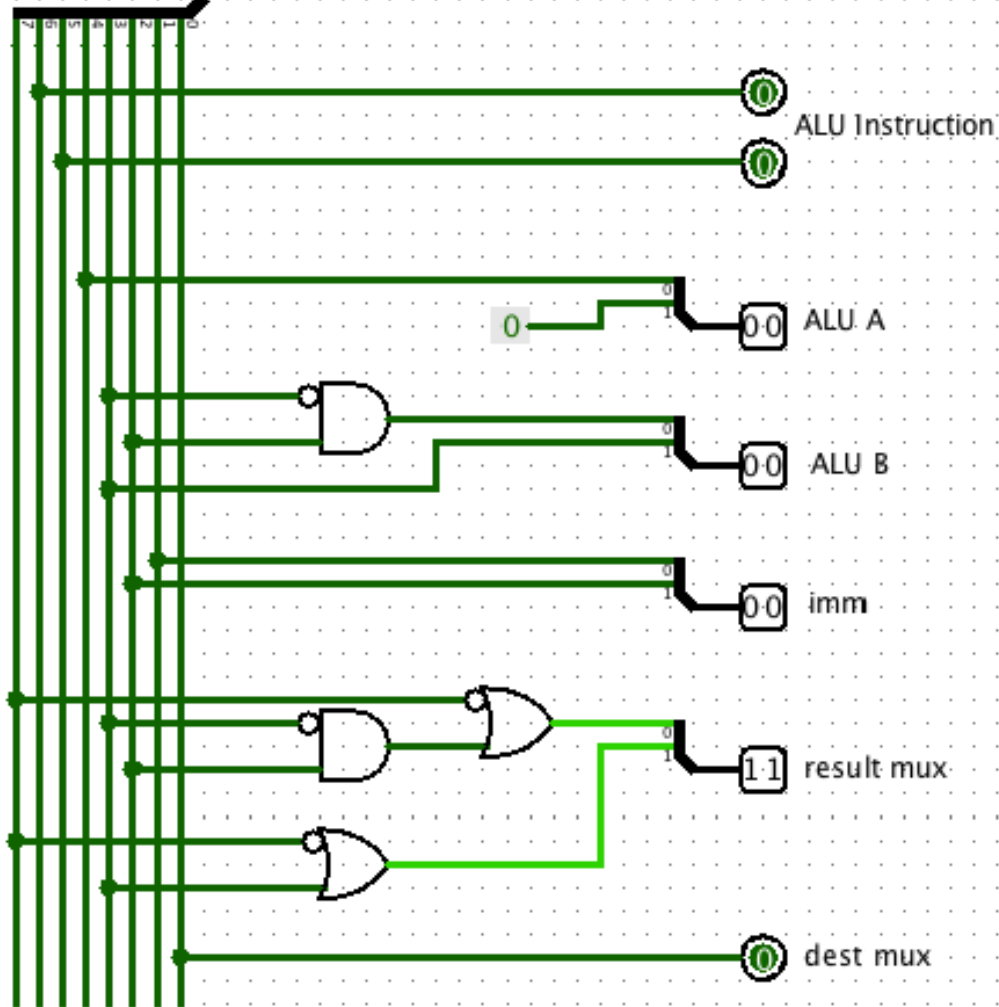

# **2-bit CPU: Version 7**

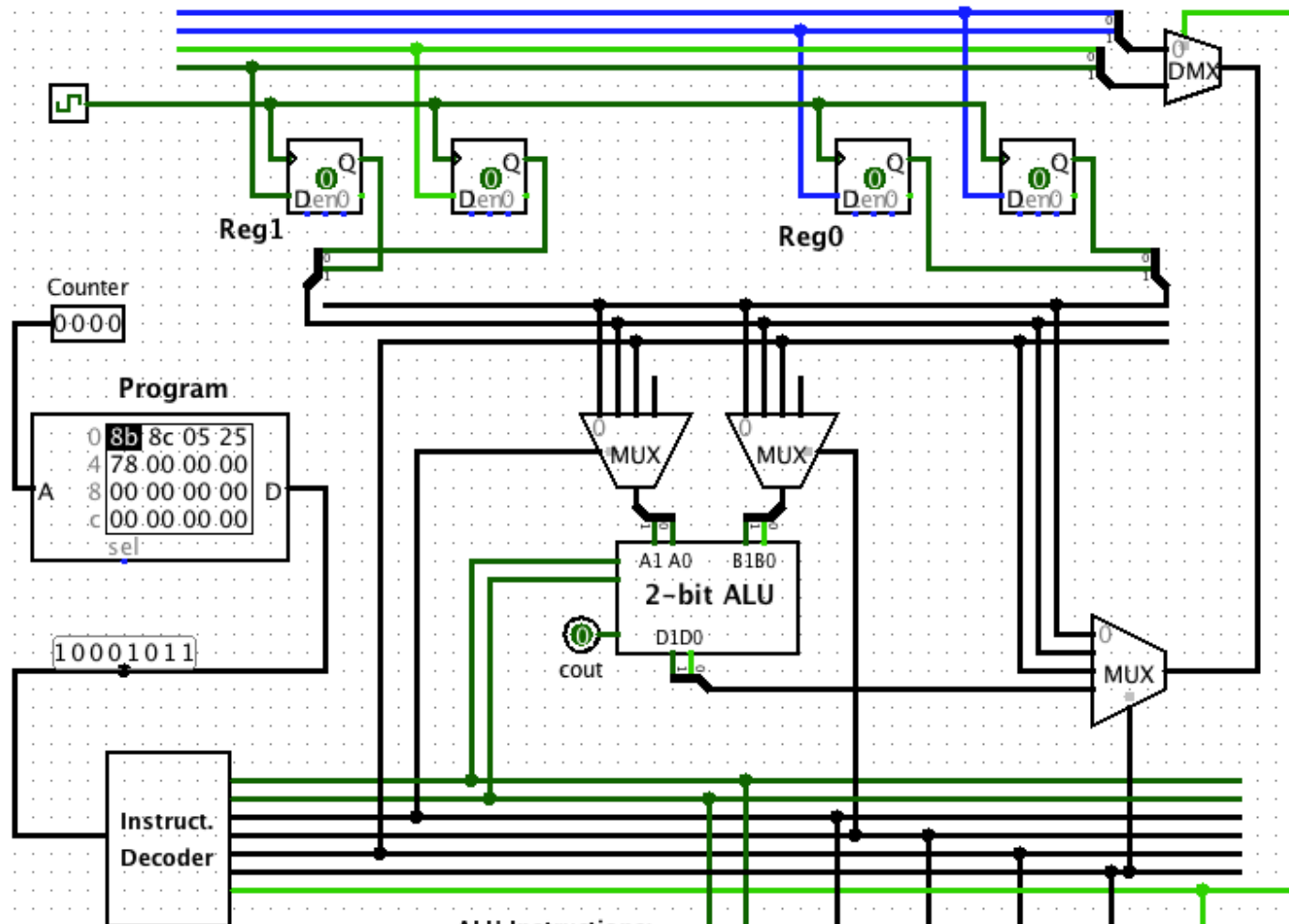**Added Program ROM which can store up to 16 instructions.**





2-bit CPU, version 7

**ALU Instructions:**

- 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT


0 0   
 00   
 10   
 01   
 10   
 1

ALU inst    ALU.A    ALU.B    imm    Res MUX    dest

**ALU MUX**                      **RES MUX**  
 00=Reg0 01=Reg1    00=Reg0 01=Reg1  
 10=imm 11=xx        10=imm 11=ALU

## **2-bit CPU: Version 8**

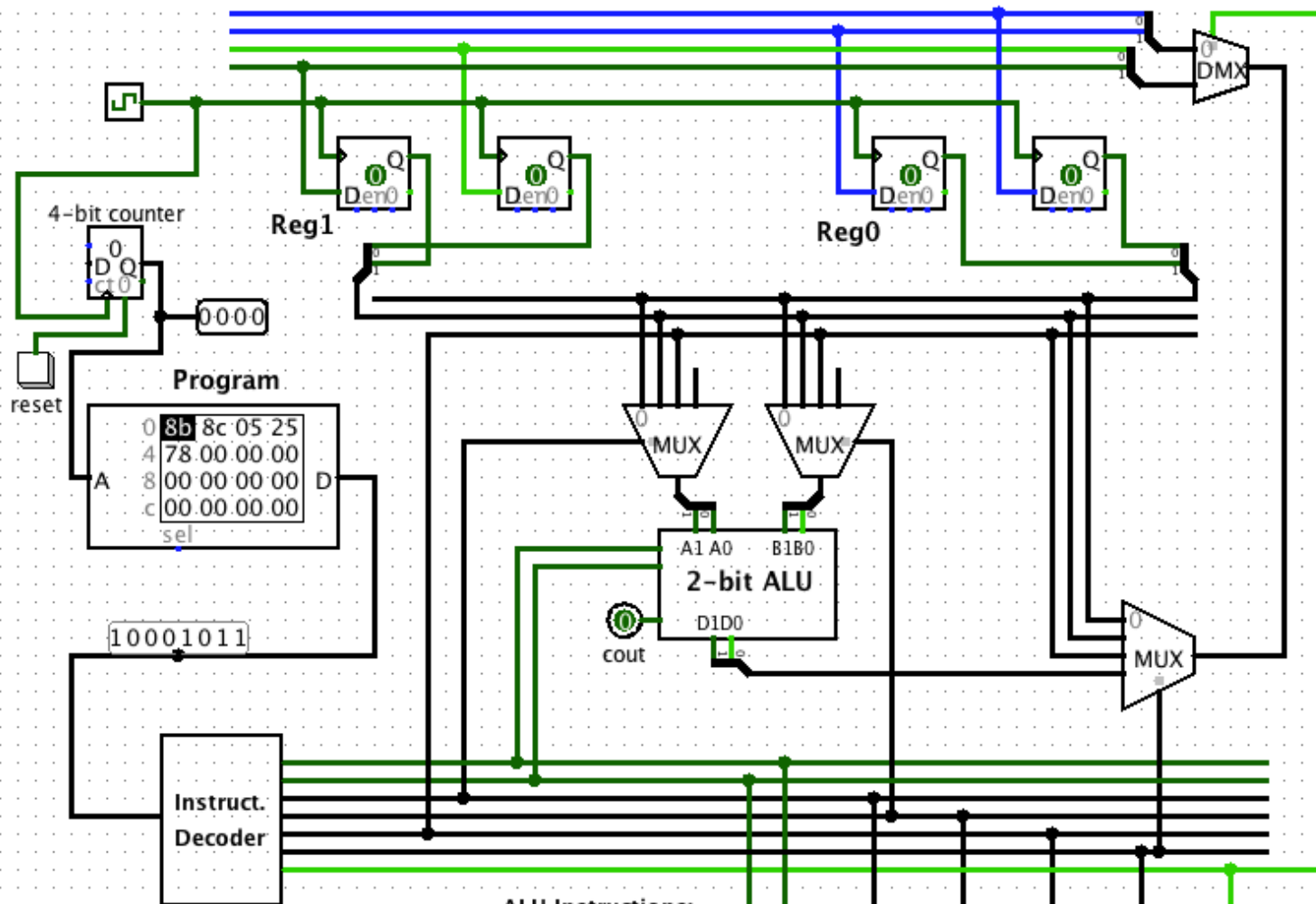**Added 4-bit counter which automatically advances Program ROM to next instruction.**



2-bit CPU, version 8

ALU Instructions:

- 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT

00    00    10    01    10    1  
 ALU inst    ALU A    ALU B    imm    Res MUX    dest


ALU MUX                      RES MUX  
 00=Reg0 01=Reg1    00=Reg0 01=Reg1  
 10=imm 11=xx        10=imm 11=ALU

# 2-bit CPU: Version 9

**Implement 4-bit counter from scratch.**




# 4-bit Counter

 

# 2-bit CPU: Version 10

**Implement Program ROM from scratch.**

# 16-bit ROM

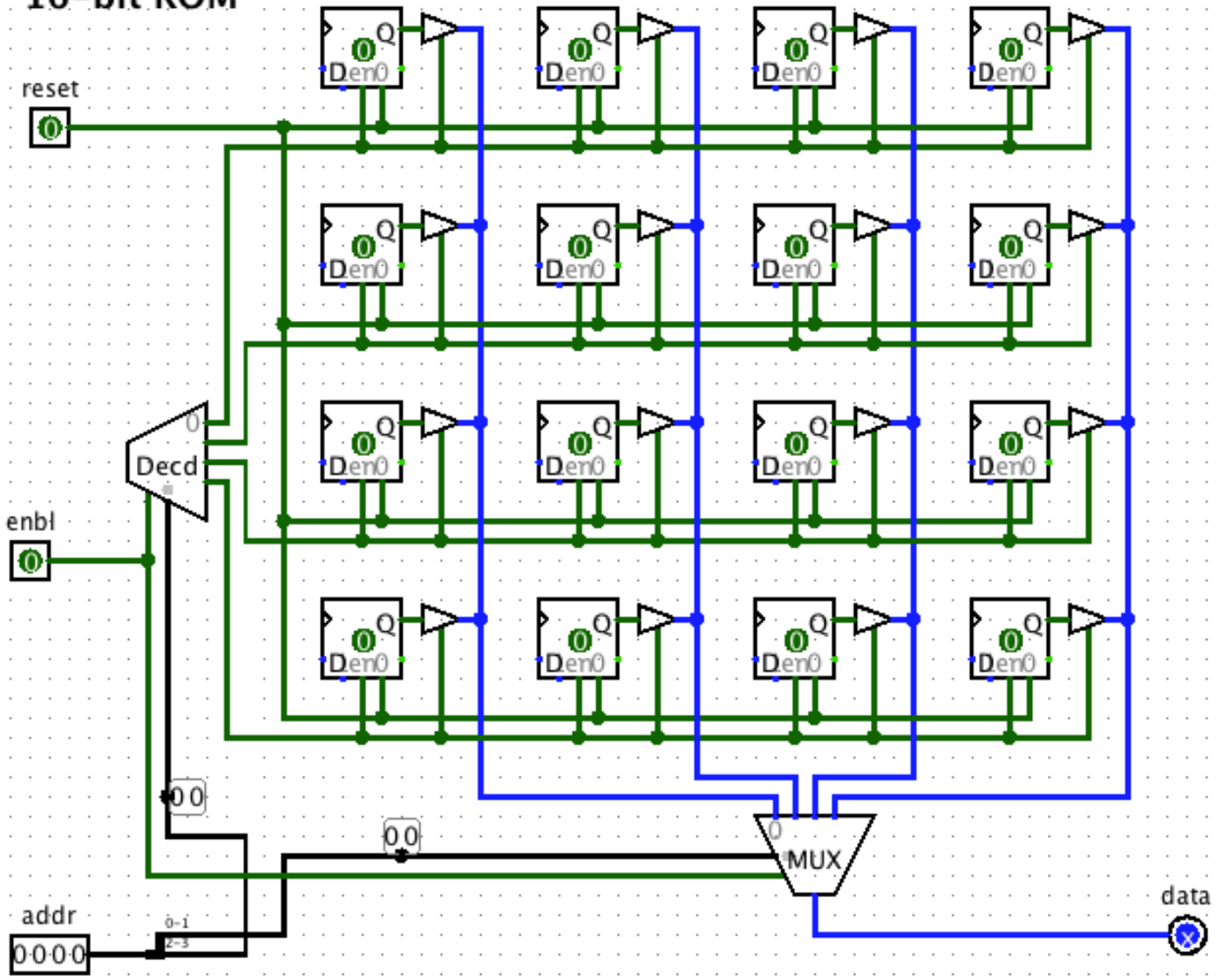

# 8 x 16-bit ROM

