

# CMSC 652

## Spring 2006

### Homework 4

**Due: Wednesday, March 8, 2006**

#### Reading Assignment:

- Douglas R. Stinson, "Cryptography: Theory and Practice," (Third edition), Chapman & Hall/CRC, (2006). Read chapters 2
- Peterson, W. Wesley, "Error-Correcting Codes, MIT Press, (1961). Read Chapter 2 (The class handout)

#### Homework:

- 1) The polynomial  $p(x) = x^2 + x + 2$  is primitive (hence, irreducible) over  $GF(3)$ . Use  $p(x)$  to construct a log/antilog table for  $GF(3^2)$ .
- 2) (a) Draw the linear sequential circuit (LSC) that multiplies by the polynomial  $h(x) = 1 + x^3 + x^6$   
(b) Draw the linear sequential circuit (LSC) that divides by the polynomial  $g(x) = 1 + x^2 + x^4 + x^6 + x^7$   
(c) Draw the linear sequential circuit (LSC) that simultaneously multiplies by  $h(x)$  and divides by  $g(x)$ .
- 3) Draw an LSC which takes as inputs polynomials  $a(x)$  and  $b(x)$ , and then produces the output  $h(x)a(x) + k(x)b(x)$ , where  $h(x)$  and  $k(x)$  are the polynomials:  
 $h(x) = 1 + x^4 + x^{10}$  and  $k(x) = x + x^2 + x^4 + x^7 + x^9$